


Brandon Wynne

Bmwynne

9/17/2015

B441

1.1: CMOS 3-Input NAND circuit

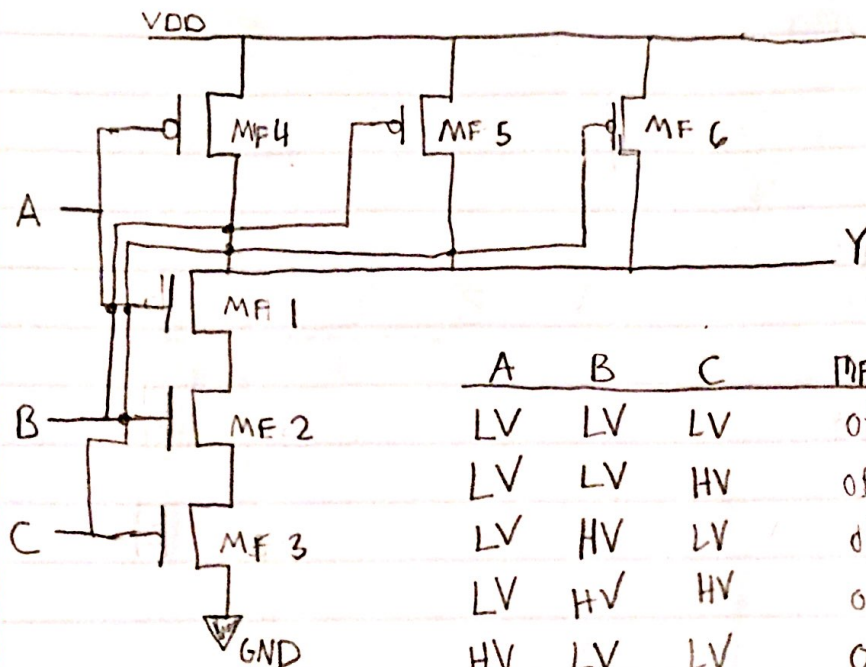


A	B	C	MF1	MF2	MF3	MF4	MF5	MF6	I	Y
LV	LV	LV	off	off	off	on	on	on	0	H
LV	LV	HV	off	off	on	on	on	off	0	H
LV	HV	LV	off	on	off	on	off	on	0	H
LV	HV	HV	off	on	on	on	off	off	0	H
HV	LV	LV	on	off	off	off	on	on	0	H
HV	LV	HV	on	off	on	off	on	off	0	H
HV	HV	LV	on	on	off	off	off	on	0	H
HV	HV	HV	on	on	on	off	off	off	0	L

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

The current is zero amps because the connection to VDD is blocked through the n/p-channel transistors at any time.

BmWyme

1.2: CMOS 3-INPUT NOR CIRCUIT

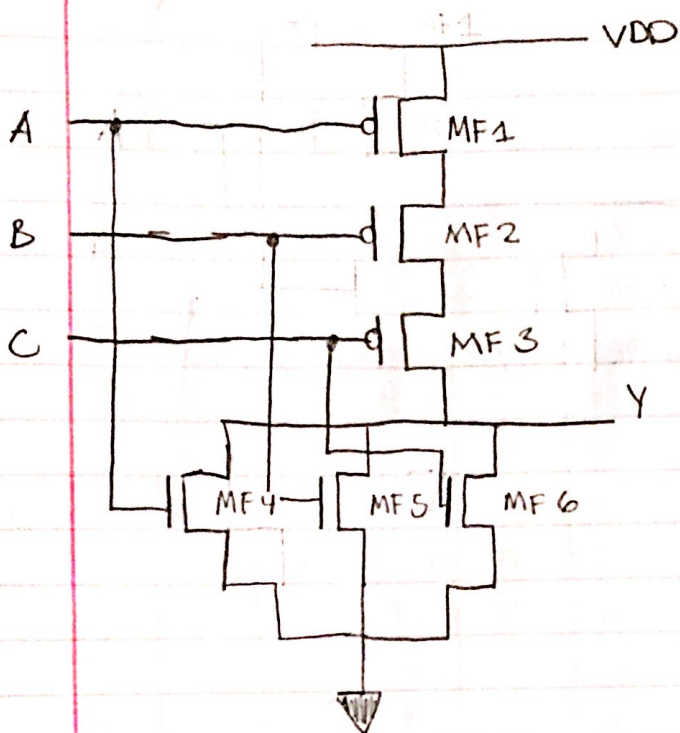



A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

A	B	C	MF1	MF2	MF3	MF4	MF5	MF6	I	Y
LV	LV	LV	ON	ON	ON	OFF	OFF	OFF	0	1
LV	LV	HV	ON	ON	OFF	OFF	OFF	ON	0	0
LV	HV	LV	ON	OFF	ON	OFF	ON	OFF	0	0
LV	HV	HV	ON	OFF	OFF	OFF	ON	ON	0	0
HV	LV	LV	OFF	ON	ON	ON	OFF	OFF	0	0
HV	LV	HV	OFF	ON	OFF	ON	OFF	ON	0	0
HV	HV	LV	OFF	OFF	ON	ON	ON	OFF	0	0
HV	HV	HV	OFF	OFF	OFF	ON	ON	ON	0	0

The current is zero amps for the same reason as the NAND circuit.

Bmwyme


Port 1.3 : CMOS Logic circuit

  

Pretty sure I'm doing this way wrong

Bmwyme

 Part 2.1: Analysis of a Combinational Logic Circuit



A	B	\bar{A}	\bar{B}	$(A \wedge \bar{B})$	$(\bar{A} \wedge B)$	$\overline{(AB + \bar{A}B)}$
T	T	F	F	F	F	T
T	F	F	T	T	F	F
F	T	T	F	F	T	F
F	F	T	T	F	F	T

Part 2.2: Analysis of a combinational logic circuit